
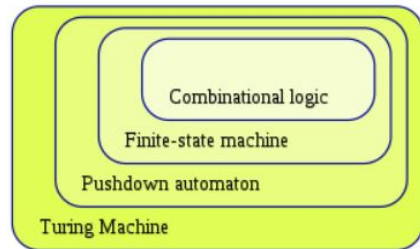


Lecture

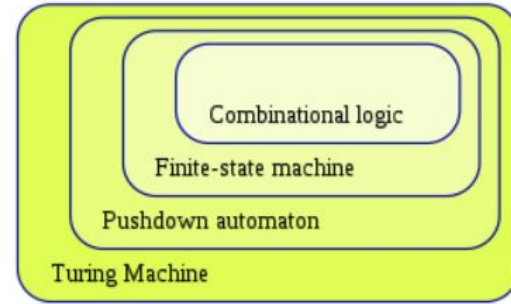

- Section 2: Digital Logic: Combinational and Sequential Circuits
 - 2 weeks followed by Quiz #2
 - 1. Boolean Algebra \Leftrightarrow Digital Circuits
 - 2. Combinational Circuits: half adder, full adder, decoders, multiplexers, BCD-7 segment
 - 3. Sequential Circuits: Latches, Registers, and Memory
 - 4. Pipeline Architecture: MIPS

Models of Computation




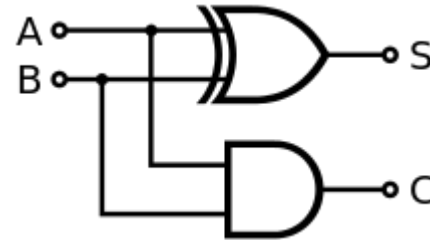
Turning Machines	Recursively Enumerable	$TM(Q, \Sigma, \Gamma, q_0, \delta)$
Linear Bounded Automata	Context Sensitive Languages	$LBA(Q, \Sigma, \Gamma, q_0, \delta)$
Pushdown Automata	Context Free Languages	$PDA(Q, \Sigma, \Gamma, \delta, q_0, z_0, F)$
Finite State Automata	Regular Expressions	$FA(Q, \Sigma, \delta, q_0, F)$
Sequential Circuits		
Combinational Logic	Boolean Algebra	

Combinational Logic

- Based upon Boolean Algebra
 - all inputs and outputs restricted to True (1) and False (0)
- Operations are restricted to: AND (*), OR (+), NOT (')
- Equivalent to Digital Logic, with gates:



- Can be used as a building blocks: 
 - XOR: $A \oplus B$ is equivalent to $(A + B) * (A' + B')$
- Example: Half-Adder



Boolean Algebra \Leftrightarrow Digital Circuits

- Circuit: a digital realization of a function: $y = f()$, $y = f(x)$, $y = f(a,b)$, ...
- Values:
 - True (T), 1, +5v
 - False (F), 0, \perp
- Functions:
 - zero inputs: clear (0), set (1)
 - one input: clear, invert, id, set

Input A	Possible Outputs			
0	0	1	0	1
1	0	0	1	1

0 0

0 1

1 0

1 1

#Inputs	Input Combinations		Output Combinations	
0	2^0	1	2^2^0	2
1	2^1	2	2^2^1	4
2	2^2	4	2^2^2	16

Two Input Functions

0010
0011
0100
1000
1001
...
1111


- 16 different functions can be created: 2^4
- List of functions:
- Definitions: [Truth Table](#):


clear	set
nor	or
\nleftarrow	\leftarrow
A'	A
\nrightarrow	\rightarrow
B'	B
neq	equiv
nand	and

A	B	0	nor	\nleftarrow	A'	\nrightarrow	B'	'equiv	nand	and	equiv	B	\rightarrow	A	\leftarrow	or	1
0	0	0	1														
0	1	0	0														
1	0	0	0														
1	1	0	0														

fold line

Boolean Algebra to Circuits

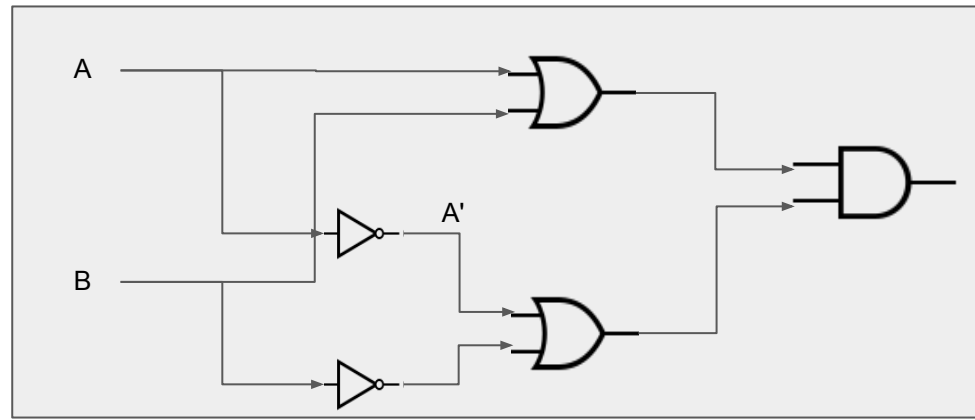- Clear: 0 \rightarrow
- Set: 1 \rightarrow
- A: A \rightarrow
- A': A \rightarrow 



- $A \oplus B: (A + B) * (A' + B')$

- $A + B:$ 

- $A * B:$ 

- $A \oplus B:$ 

A	B	xor	and	or
0	0	0	0	0
0	1	1	0	1
1	0	1	0	1
1	1	0	1	1

Truth Table Reduced to a Circuit

- Generate a circuit as a sum of products
- Values: 0, 1
- Functions: Not ('), And (*), Or (+)
- Example: Implication: $A \leftarrow B$
 - ~~If A is true then B must also be true!~~
- Consider the Truth Table
- Evaluate each row:
- Combine all rows that are true
 - Output = ~~$A'B' + A'B + AB$~~
 - Output = $A'B' + AB' + AB$

A	B	Output		
0	0	1		A'B'
0	1	0		A'B
1	0	1		AB'
1	1	1		AB

Bob : (ABC')'

More Complex Reduction

A	B	C	Bob	Sally
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

A'B'C'
A'B'C
A'BC'
A'BC
AB'C'
AB'C
ABC'
ABC


Circuit to Boolean Algebra

- One Formula for each output
- Work Backwards, Divide and Conquer!

$$\text{Output} = (x + y) * (j + k)$$

$$\text{Output} = (A + B) * (G' + H')$$

$$\text{Output} = (A + B) * (A' + B')$$

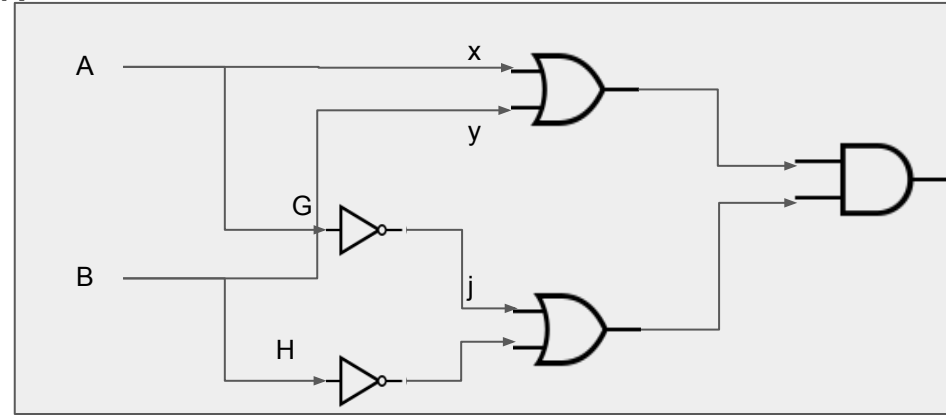

$$3 * (5 + 6) == 3 * 5 + 3 * 6$$

Simplification \Leftrightarrow Minimization

- The above method can yield large circuits
 - Unnecessary large circuits, like programs, are bad:
 - require larger chips
 - require more time to evaluate
- Two approaches:
 - Use algebraic properties to rewrite the formulas
 - Use Karnaugh maps to visualize patterns of simplification
- Algebraic Properties:
 - associative, commutative, distributive
 - complement ($A * A' \Leftrightarrow 0$), De Morgan's law : $A' * B' \Leftrightarrow (A + B)'$
 - $A' + A \Leftrightarrow 1$
- Example
 - $R = A' * B + A * B$

$$R = A' * B + A * B$$

$$R = B * A' + B * A$$

$$R = B * (A' + A)$$

$$R = B * 1$$

$$R = B$$

Karnaugh Map

- Truth Table: $R = A'B + A*B$

A	B	Output
0	0	0
0	1	1
1	0	0
1	1	1

'(A'B)'
A'B
'(AB)'
AB

- Karnaugh Map: for two variables

		B	
		0	1
A	0	0	1
	1	0	1

- Find groups that contain only 1s
- Group size must be in power of two (1, 2, 4, 8)
- $R = B$

3-Variable Karnaugh Map

A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

		BC			
		00	01	11	10
A	0	1	1	0	0
	1	1	1	1	0


00
01
10
11

$$\text{output} = B' + AC$$

$$\text{output} = B' + ABC$$

Rules for K-maps

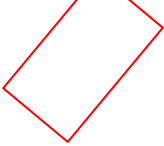- Groups only contains 1s
- Group size must be a power of two
- Groups must be rectangular, no diagonals
- Groups can overlap
- Groups can wrap
- For Minimization:
 - Use the largest group
 - Use the fewest number of groups
 - But all 1s must be contained in at least one group.



		BC			
		00	01	11	10
A	0	0	1	1	1
	1	1	0	0	1

$$\text{output} = A'C + AB' + A'BC'$$

		BC				BC			
		00	01	11	10	00	01	11	10
A	0	1			1	1			1
	1	1			1	1			1