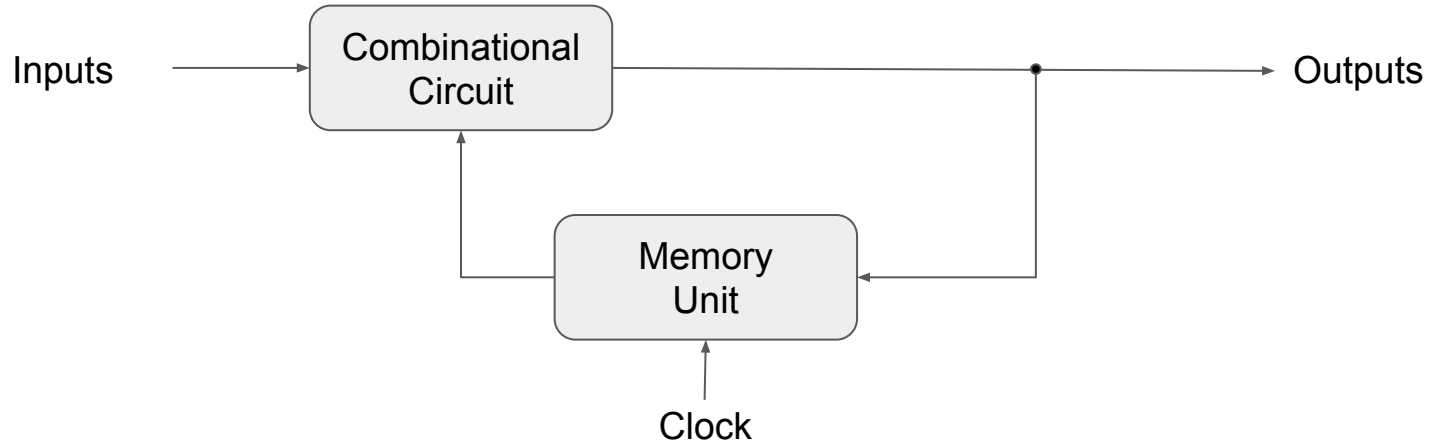


Lecture:

- Last Time:
 - Control Lines and the CPU
 - On-Off Switch
 - Decoder to select which register.
 - Mux to select ALU Output
 - CPU Overview: Data with some control lines.
 - High-level memory schematic
 - Questions
- Today:
 - Sequential Circuits: clocks, latches, and flip/flops:
 - CPU Control: PC/IR
 - MIPS pipeline architecture
- Next: Onto Assembly Language Program:
 - Assembly Level Programming
 - Three-address code
 - MIPS assembly code

Sequential Circuit

- Sequential circuit infuses a memory component
- Memory serves as both input and output




- A clock is used to trigger the update of the memory unit

Clock: an electronic device

- Generates a periodic signal
- Forms a square wave
- Frequency = $1 / (\text{Time Period})$
- Used as a control signal to active parts of a circuit

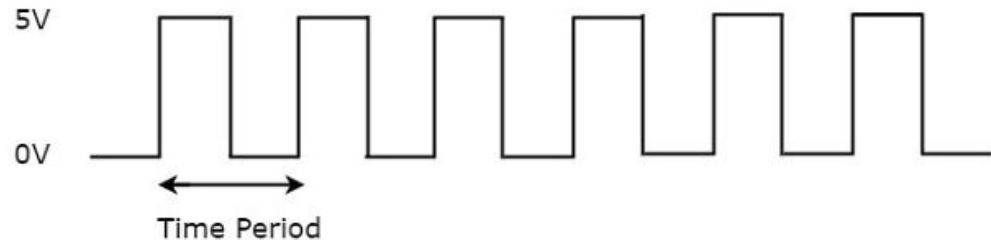
- Types of Triggers:
 - Level Trigger
 - Edge Trigger
- Level of Triggers:
 - Positive Level (Hi)
 - Negative Level (Lo)



* Recall you can active some GUI elements on a mouse click, mouse press, **OR** a mouse release

SR Latch

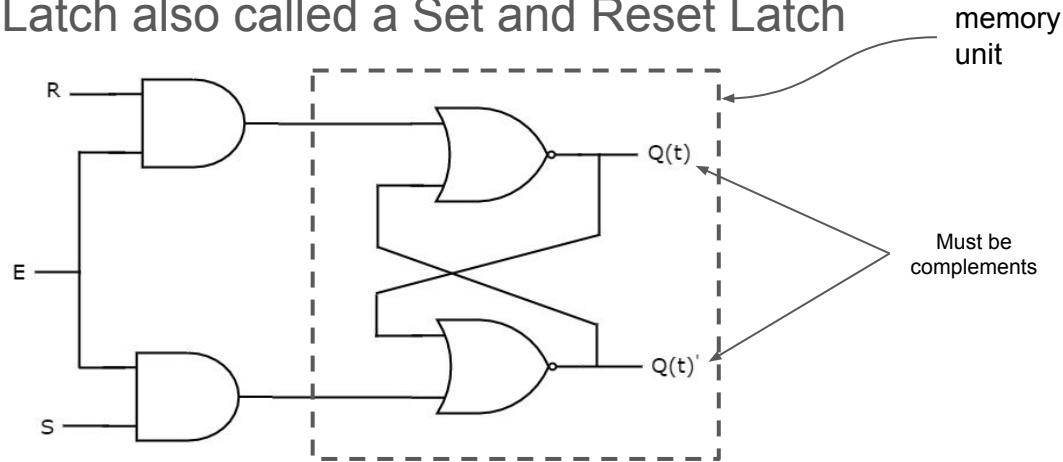- SR Latch also called a Set and Reset Latch




- Functionally:
 - E : Used to enable the circuit: i.e., trigger an update
 - R : Used to clear (reset) the memory unit
 - S : Used to set the memory unit

S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	-

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

SR Latch: Set at (1,0)

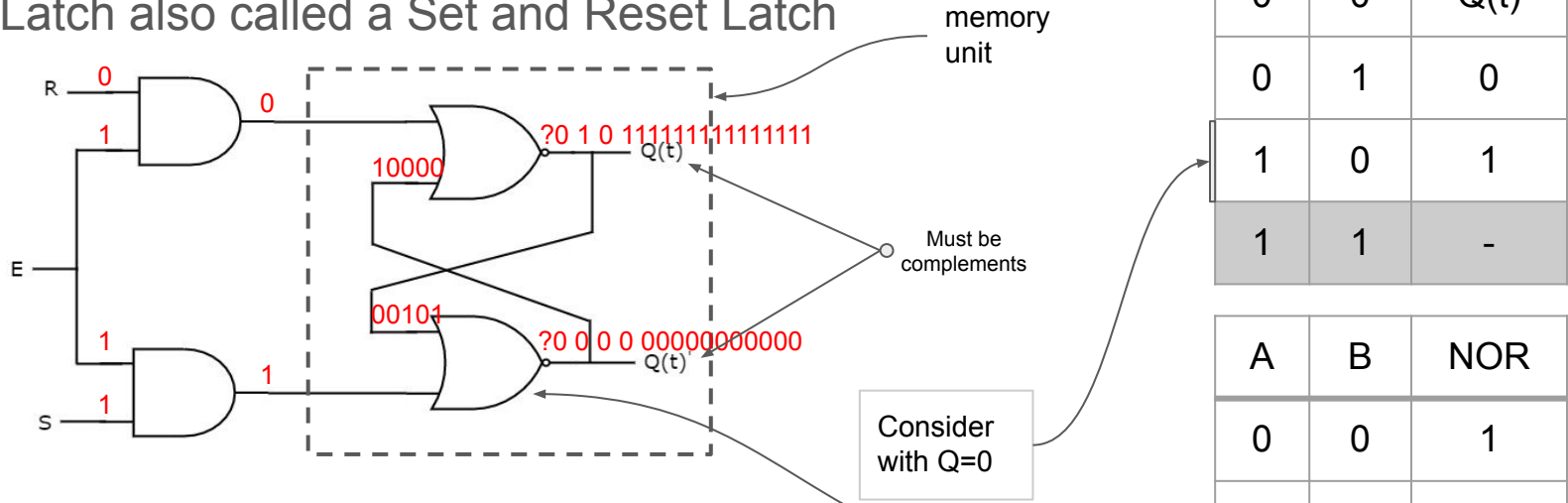- SR Latch also called a Set and Reset Latch




- Functionally:

- E: Used to enable the circuit: i.e., trigger an update
- R: Used to clear (reset) the memory unit
- S: Used to set the memory unit

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

D Latch: Data Latch

- Forces S & R to be complements

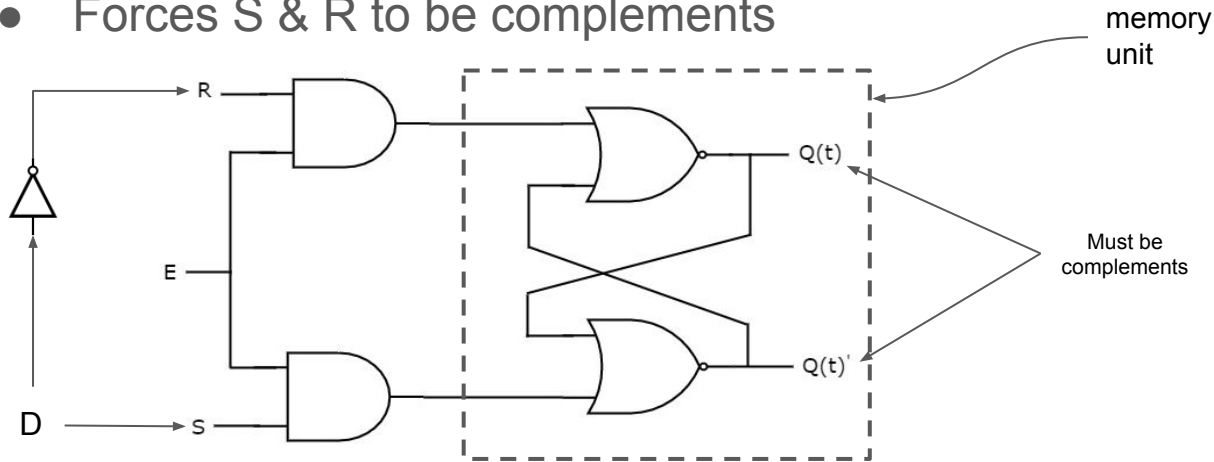

- Functionally:


- E: Used to trigger the memory unit, i.e., perform a write
- D': Used to clear (reset) the memory unit
- D: Used to set the memory unit

E	D	$Q(t+1)$
0	0	$Q(t)$
0	1	$Q(t)$
1	0	0
1	1	1

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Latches and Flip-Flops

Logically the same!

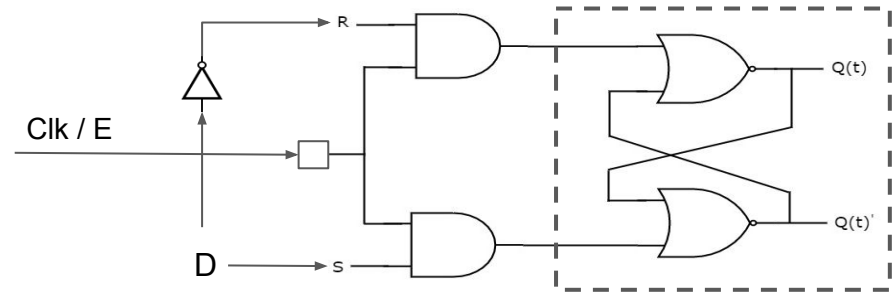


Differences:

- Latches:
 - RS Latch
 - D Latch
 - JK Latch
 - T Latch
- Flip-Flop:
 - RS Flip-Flop
 - D Flip-Flop
 - JK Flip-Flop
 - T Flip-Flop

Latches	Flip-flops
Different underlying technology is used	
Uses a enable signal	Uses a clock signal
Level triggered	Edge triggered
Uses a enable signal	Uses a clock signal
Consumes less power	Consumes more power
Faster	Slower
Used for transitioning (Consider a lock, e.g., at the Panama Canal.)	Used as storage

4-bit Register

- D Flip-Flop

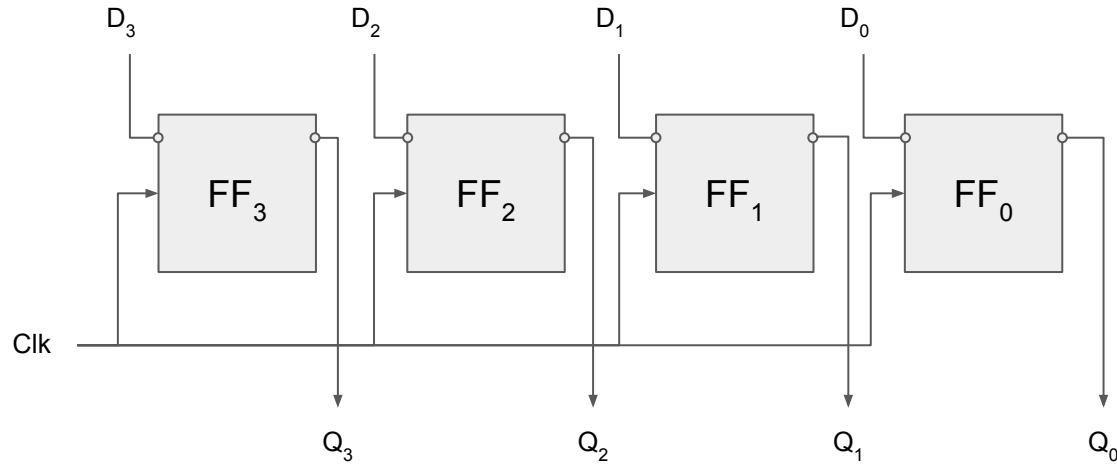

What do we have now?

1. Basic understanding of circuitry and its relationship to Boolean algebra.
2. Knowledge of "state" and how it is used to build registers and memory units
3. Recognize how we can build components to build a CPU
 - ALU, registers, decoders, multiplexers, etc., as well as main memory.
4. Almost ready for the abstract all this away in favor of an ISA
Instruction Set Architecture

But first, let's put all the pieces together to create the MIPS microarchitecture!

MIPS: CPU Control

- The CPU executes specific circuitry in stepwise fashion
 - Fetch, Decode, Execute, Mem Access, WriteBack
 - Unnamed Latches are used between each phase
- PC: Program Counter
 - Holds the address of the NEXT instruction to be executed
 - The PC is increment by 1 instruction, i.e., 4 bytes, every cycle
 - Each instruction requires 4 bytes to encode
- IR: Instruction Register
 - Stores the current instruction to be executed
 - Each instruction is decoded (electronically) to trigger operations in the circuitry
 - Three types of encodings: R, I, J
 - Operations involving the Registers and ALU
 - Operations involving ImmEDIATE values
 - Operations involving Jumps and Branches

```
.text → int f( int a) {  
    int x;  
    int y;  
    int b;  
  
    x = a + 2;  
    b = ( x > 0 )  
    if ( b )  
        x = x + b;  
    y = x * 3;  
    y = y << 2 ;  
  
    return y;  
}
```

MIPS Instruction Set

- Jump and Branch examples:

- `jal address` \Leftrightarrow function call
- `jr rs` \Leftrightarrow function return
- `beq rs, rt, imm` \Leftrightarrow if (`rs == rt`) goto `imm`


- ALU examples:

- `add rd, rs, rt` \Leftrightarrow `rd = rs + rt`
- `ori rd, rs, imm` \Leftrightarrow `rd = rs | imm`

- Memory examples:

- `la rs, label` \Leftrightarrow
- `lb rt, imm(rs)` \Leftrightarrow `rt = SignExt(M1 [rs + imm])`
- `lwu rt, imm(rs)` \Leftrightarrow `rt = M4 [rs + imm]`
- `sh rt, imm(rs)` \Leftrightarrow `M2 [rs + imm] = rt`

Encoding: Instruction Register

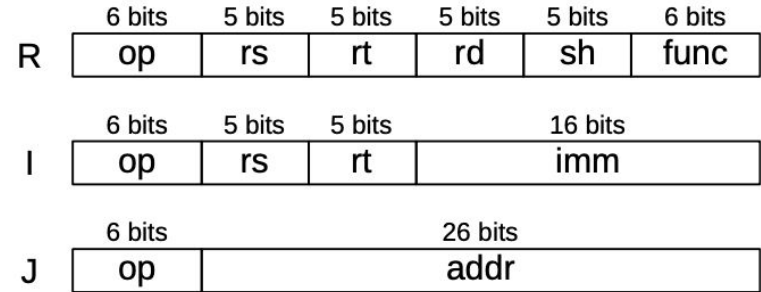

→ `ADD $r0, $r2, $r3`

→ `ORI $r0, $r2, 5`

→ `$rs = &A`


→ `$rt = (char) A[0]`

→ `$rt = (unsigned word) (A[16])`

→ `A[32] = (half) $rt`

MIPS Pipeline Architecture

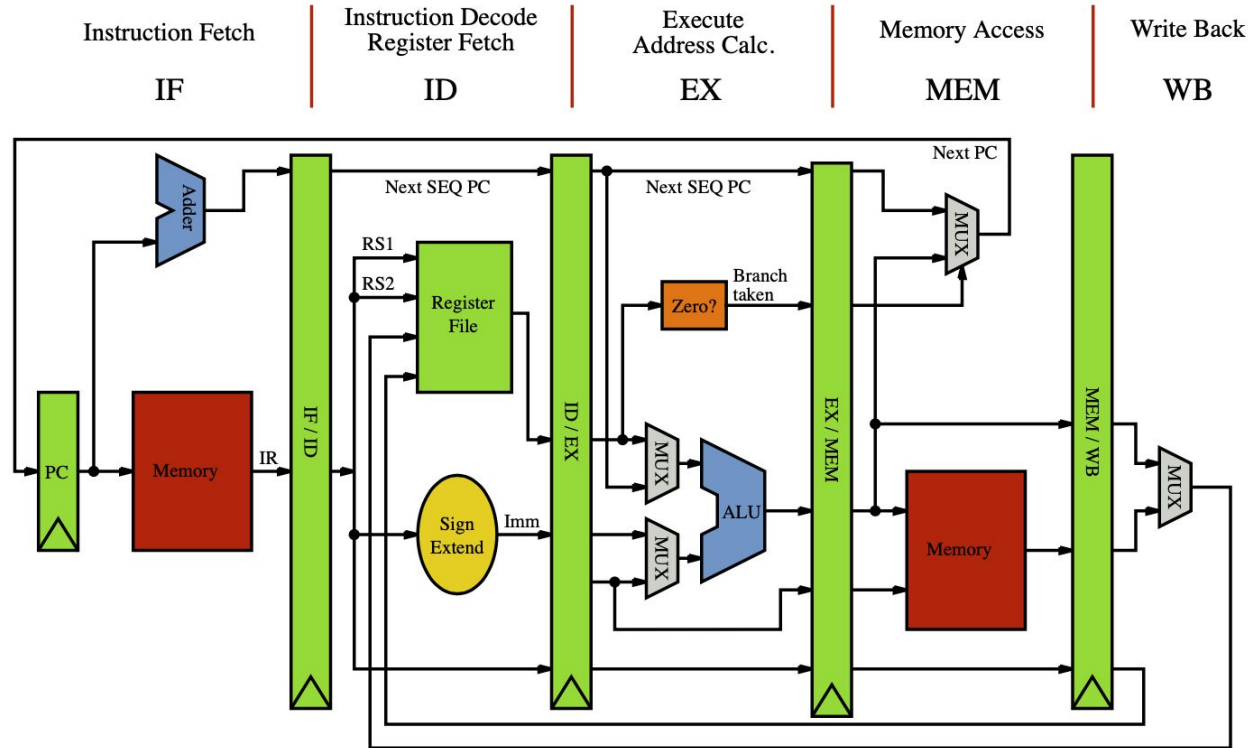- Fives Stages →
- Major Sections:
 - PC update
 - ALU
 - Memory
- PC update
 - next instruction
 - branch
 - (PC + 4) / ALU mux
- ALU
 - imm / register mux
 - register / PC mux
- Memory
 - Harvard Model
 - ALU / memory mux



Instruction Fetch

Instruction Decode
Register FetchExecute
Address Calc.

Memory Access

Write Back

IF

ID

EX

MEM

WB

